 


# Digital Fundamentals


ELEVENTH EDITION



## CHAPTER 1


### Introductory Concepts

# Graph of an analog quantity

 


Sampled-value representation (quantization) of analog quantity.

 
Each dot can be digitized by representing by series of 1s and 0s.



# A basic audio public address system

 


# Basic block diagram of a CD player

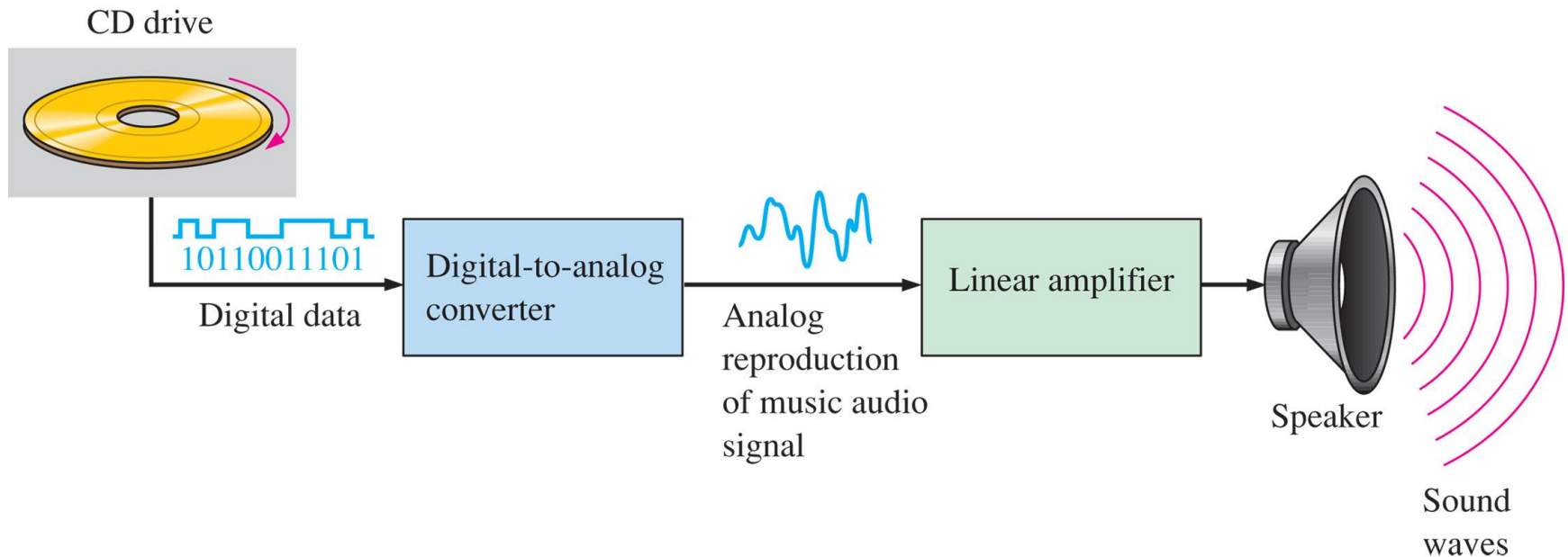


# Binary Digits

**HIGH = 1   and   LOW = 0**

 
# Logic level ranges of voltage for a digital circuit



# Ideal pulses

 


(a) Positive-going pulse

 


(b) Negative-going pulse



# Nonideal pulse characteristics

 

# Examples of digital waveforms

 


(a) Periodic (square wave)



(b) Nonperiodic

$$f = \frac{1}{T}$$

$$T = \frac{1}{f}$$

 


$$\text{Duty cycle} = \left( \frac{t_W}{T} \right) 100\%$$

# Example

A portion of a periodic digital waveform is shown in Figure 1–10. The measurements are in milliseconds. Determine the following:

- (a) period      (b) frequency      (c) duty cycle

 

**FIGURE 1–10**


## Solution

- (a) The period ( $T$ ) is measured from the edge of one pulse to the corresponding edge of the next pulse. In this case  $T$  is measured from leading edge to leading edge, as indicated.  $T$  equals **10 ms**.


(b)  $f = \frac{1}{T} = \frac{1}{10 \text{ ms}} = \mathbf{100 \text{ Hz}}$

(c) Duty cycle  $= \left( \frac{t_W}{T} \right) 100\% = \left( \frac{1 \text{ ms}}{10 \text{ ms}} \right) 100\% = \mathbf{10\%}$

 
## Example of a clock waveform synchronized with a waveform representation of a sequence of bits




# Example of a timing diagram

 
 
# Illustration of serial and parallel transfer of binary data



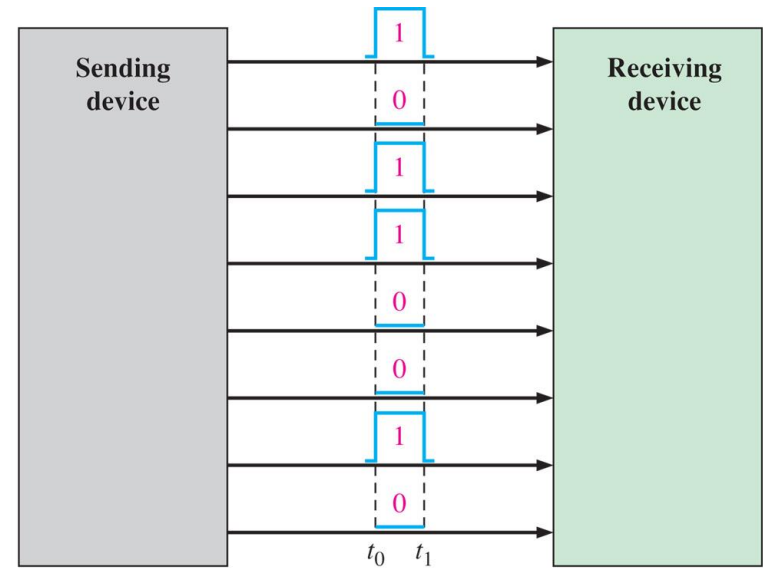
(a) Serial transfer of 8 bits of binary data. Interval  $t_0$  to  $t_1$  is first.



(b) Parallel transfer of 8 bits of binary data. The beginning time is  $t_0$ .

# Example

 - (a) Determine the total time required to serially transfer the eight bits contained in waveform *A* of Figure 1–14, and indicate the sequence of bits. The left-most bit is the first to be transferred. The 1 MHz clock is used as reference.
- (b) What is the total time to transfer the same eight bits in parallel?





# Solution

- (a) Since the frequency of the clock is 1 MHz, the period is

$$T = \frac{1}{f} = \frac{1}{1 \text{ MHz}} = 1 \mu\text{s}$$

It takes 1  $\mu\text{s}$  to transfer each bit in the waveform. The total transfer time for 8 bits is

$$8 \times 1 \mu\text{s} = 8 \mu\text{s}$$




The left-most bit is the first to be transferred.

- (b) A parallel transfer would take 1  $\mu\text{s}$  for all eight bits.

# Basic Logic Functions

- ◆ Define the NOT function
- ◆ Define the AND function
- ◆ Define the OR function


# The basic logic functions and symbols

 

NOT





AND


 


OR





# The NOT function

  


# The AND function

  


# The OR function

    

# The comparison function

 


(a) Basic magnitude comparator

 


(b) Example:  $A$  is less than  $B$  ( $2 < 5$ ) as indicated by the HIGH output ( $A < B$ )

# The addition function

 

(a) Basic adder

 


(b) Example: A plus B ( $3 + 9 = 12$ )



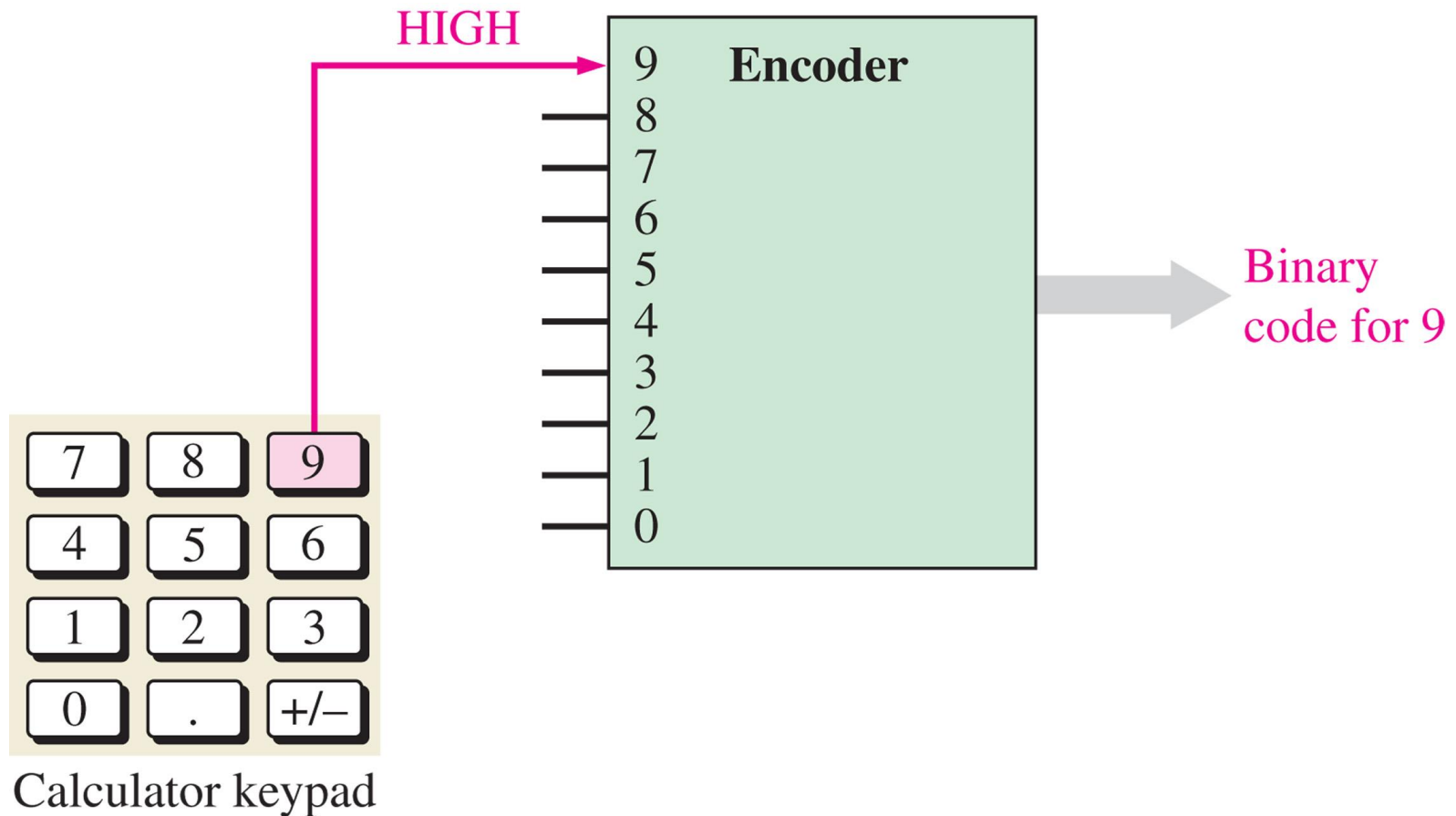
# The Arithmetic Functions

Addition,  
Subtraction,  
Multiplication,  
Division


An encoder used to encode a calculator keystroke into a binary code



 A decoder used to convert a special binary code into a 7-segment decimal readout


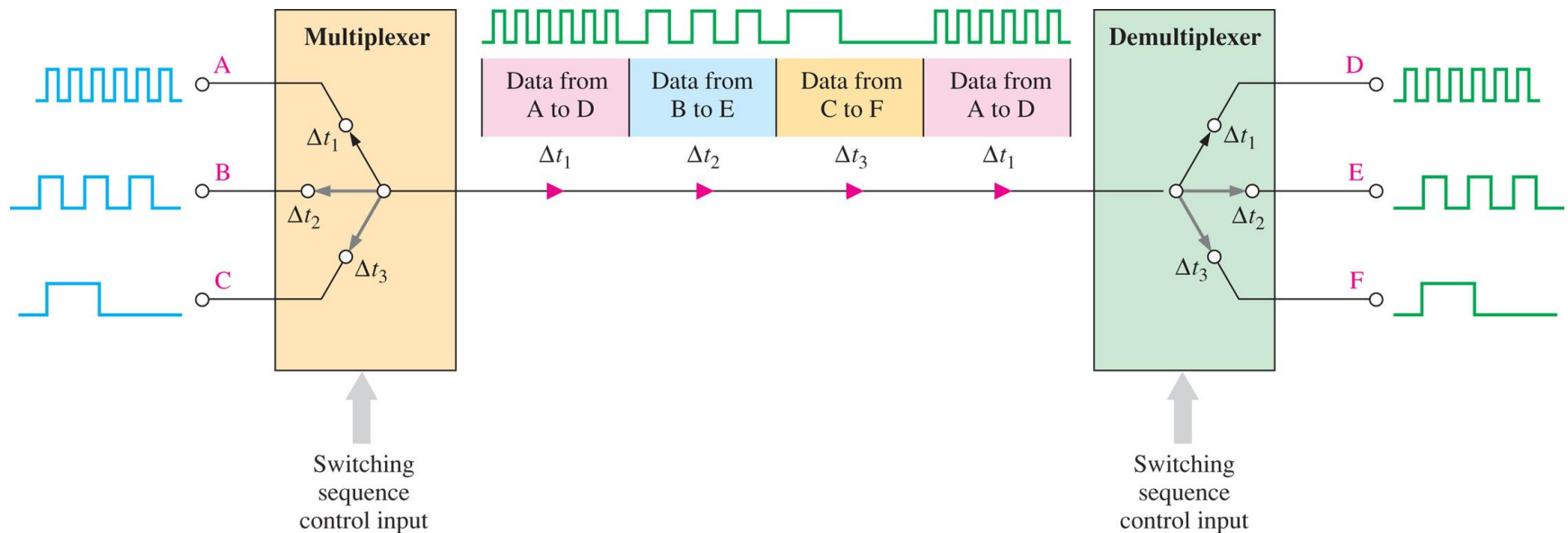
# Illustration of a basic multiplexing/demultiplexing application




# Example of the operation of a 4-bit serial shift register

Each block represents one storage “cell” or flip-flop

Serial bits  
on input line

0101 →

 

Initially, the register contains only *invalid* data or all zeros as shown here.

010 →




First bit (1) is shifted serially into the register.

01 →




Second bit (0) is shifted serially into register and first bit is shifted right.

0 →

 

Third bit (1) is shifted into register and the first and second bits are shifted right.


→

 


Fourth bit (0) is shifted into register and the first, second, and third bits are shifted right. The register now stores all four bits and is full.

## Example of the operation of a 4-bit parallel shift register

Parallel bits  
on input lines

 

 Initially, the register is empty,  
containing only nondata zeros.




All bits are shifted in and  
stored simultaneously.

# Memories


Semiconductor Memories,  
Magnetic Memories,  
Optical Memories
 
# Illustration of basic counter operation




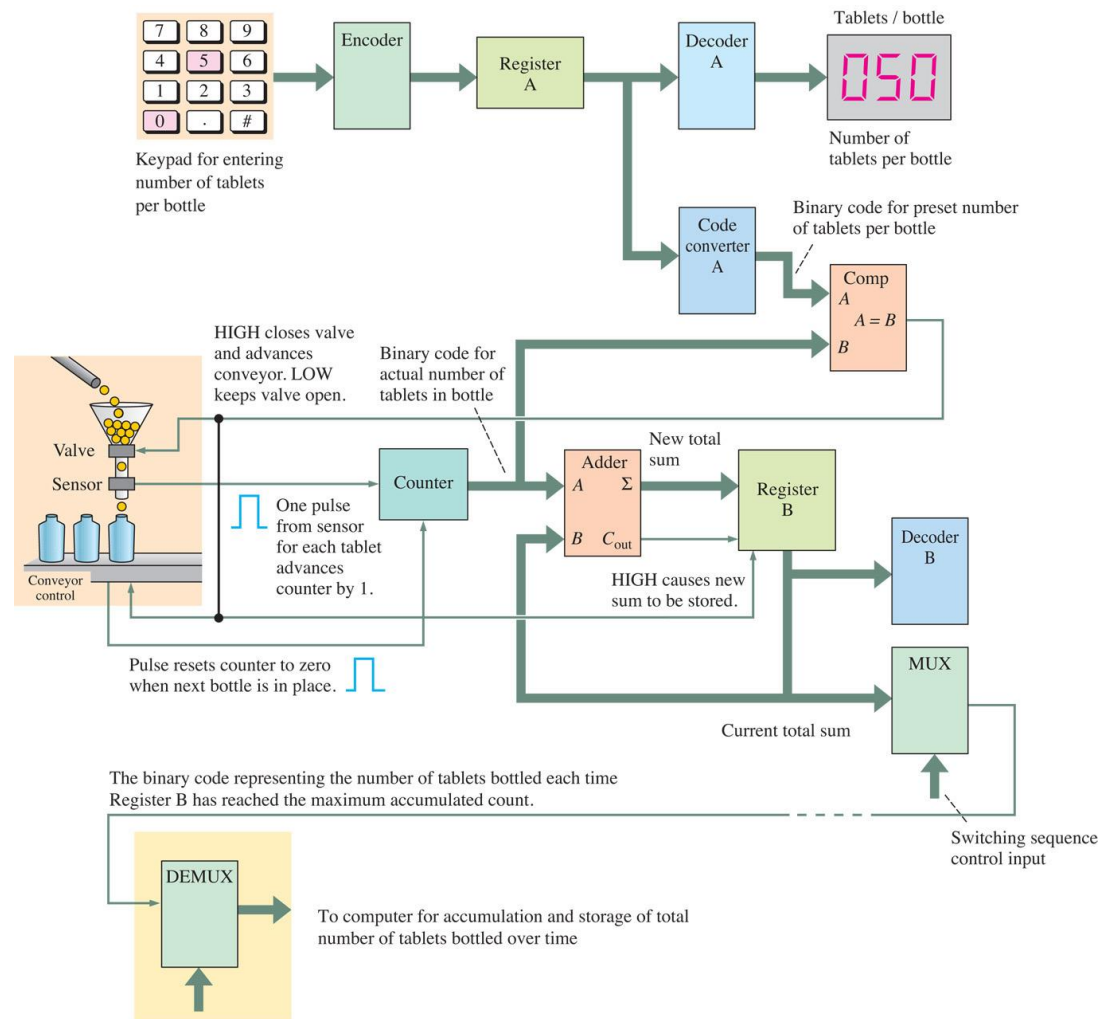
# Block diagram of a tablet-bottling system



# Programmable logic hierarchy

